

Analog Integrated Systems Design


Lecture 07 Basics of Sample & Hold Circuits

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University



Sampling

 - ❑ Converts a continuous time (CT) signal to a discrete time (DT) signal
 - The result is a sequence of samples
- ❑ The sampling instants are defined by a clock signal
- ❑ The clock signal controls an electronic switch (e.g., MOS transistor)
- ❑ The sampled signal is stored as a voltage on a capacitor




Track & Hold (T/H)

  - ❑ What we implement practically is a T/H not a S/H
 - Switch closed (ON): Track mode
 - Switch open (OFF): Hold mode
- ❑ But we sometimes refer to it as S/H




T/H vs S/H

 


Tracking Bandwidth (TBW)

 - ❑ MOS technology is naturally suitable for implementing T/H
- ❑ The lowpass network determines the tracking bandwidth
- ❑ Tracking bandwidth determines how promptly V_o can follow V_i
- ❑ Signal-dependent R_{on} \rightarrow signal-dependent TBW \rightarrow distortion
 - Not a concern if TBW is sufficiently large
 - $TBW \gg f_{in}$, depending on the target accuracy



 
$$R_{on}^{-1} = \mu C_{ox} \frac{W}{L} (V_{DD} - V_{th} - V_i)$$



$$TBW = 1/(R_S + R_{on})C_S$$

T/H Speed-Accuracy Trade-off

 - ❑ Short L , large W , large V_{ov} , and small V_i help reduce R_{on} \rightarrow More speed
- ❑ But large W and V_{ov} (large Q_{ch}) increase T/H errors \rightarrow Less accuracy



$$\tau = \frac{1}{\text{TBW}} = (R_S + R_{on})C_S$$

$$R_{on} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{DD} - V_{th} - V_i)} = \frac{L^2}{\mu C_{ox} W L (V_{DD} - V_{th} - V_i)} = \frac{L^2}{\mu Q_{ch}}$$


Acquisition Time (t_{acq})

- Assume linear settling of first order system

$$V(t) = V_i + (V_f - V_i)(1 - e^{-\frac{t}{\tau}})$$
$$T = \tau \ln \left(\frac{V_f - V_i}{V_f - V(T)} \right) = \tau \ln \left(\frac{\Delta V}{\epsilon} \right)$$

- If $\Delta V = FS$ and $\epsilon < 1LSB = \frac{FS}{2^N}$

$$t_{acq} = \tau \ln(2^N) = 0.69N\tau$$

 


$$\tau = \frac{1}{\text{TBW}} = (R_S + R_{on})C_S$$

Accuracy	t_{acq}
1% (7b)	$\geq 5\tau$
0.1% (10b)	$\geq 7\tau$
0.01% (13b)	$\geq 9\tau$



Ideal T/H

 - ❑ Sufficient tracking bandwidth \rightarrow negligible tracking error
- ❑ Well-defined sampling instant (asserted by clock rising/falling edge)
- ❑ Zero track-mode and hold-mode offset errors



T/H Errors (1)

  - ❑ Pedestal step:
 - Switch charge injection (CI)
 - Clock feedthrough (CF)
- ❑ Droop: Due to leakage. Dictates min sample rate. More leakage in deep submicron (DSM) nodes.
- ❑ Hold-mode feedthrough (C_{feed}): Usually negligible.





T/H Pedestal Step

$$V_{pedestal} = \frac{C_{ped}\Delta V_{gate} + Q_{gate}/2}{C_{hold}} = -\frac{WC_{olap}V_{DD} + WLC_{ox}(V_{DD} - V_{in} - V_{T,N})/2}{C_{hold}}$$

- ❑ Offset and gain error components
- ❑ Nonlinear error component:
 - V_T depends nonlinearly on $V_{in} \rightarrow$ Distortion
- ❑ CF and CI sensitive to source impedance, C_H , and clock rise/fall time
- ❑ CF can be simulated by SPICE
 - But CI cannot be accurately simulated with lumped transistor models

Pedestal Step Edge Rate Dependence

  - ❑ Slow turn-off is good for CI and CF
 - But more sensitive to jitter and signal dependent aperture delay (more later)



	Clock feedthrough	Charge injection
Fast turn-off	$\Delta V = -\frac{C_{gs}}{C_{gs} + C_S} V_{DD}$	$\Delta V = -\frac{C_{ox} WL (V_{DD} - V_{th} - V_{in})}{2(C_{gs} + C_S)}$
Slow turn-off	$\Delta V = -\frac{C_{gs}}{C_{gs} + C_S} (V_{in} + V_{th})$	$\Delta V = 0$

Top-Plate T/H Pedestal Error

Slow turn-off:

$$V_o = (1 + \epsilon) \cdot V_i + V_{os}$$

$$V_o = \left(1 - \frac{C_{gs}}{C_{gs} + C_S} \right) \cdot V_i - \frac{C_{gs}}{C_{gs} + C_S} V_{th}$$

Fast turn-off:

$$V_o = (1 + \epsilon) \cdot V_i + V_{os}$$

$$V_o = \left(1 + \frac{1}{2} \frac{C_{ox} WL}{C_{gs} + C_S} \right) \cdot V_i - \left[\frac{C_{gs}}{C_{gs} + C_S} V_{DD} + \frac{1}{2} \frac{C_{ox} WL}{C_{gs} + C_S} (V_{DD} - V_{th}) \right]$$

Watch out for nonlinear errors!

T/H Speed-Accuracy Trade-off

- ❑ Technology scaling improves T/H performance!


Pedestal error: $\Delta V \approx \frac{1}{2} \frac{Q_{\text{ch}}}{C_S}$

TBW: $\text{TBW} \approx \frac{1}{R_{\text{on}} C_S} = \frac{\mu Q_{\text{ch}}}{L^2 C_S}$

$$\frac{\Delta V}{\text{TBW}} \approx \frac{1}{2} \frac{Q_{\text{ch}}}{C_S} \cdot \frac{L^2 C_S}{\mu Q_{\text{ch}}} = \frac{L^2}{2\mu}$$



Dummy Switches

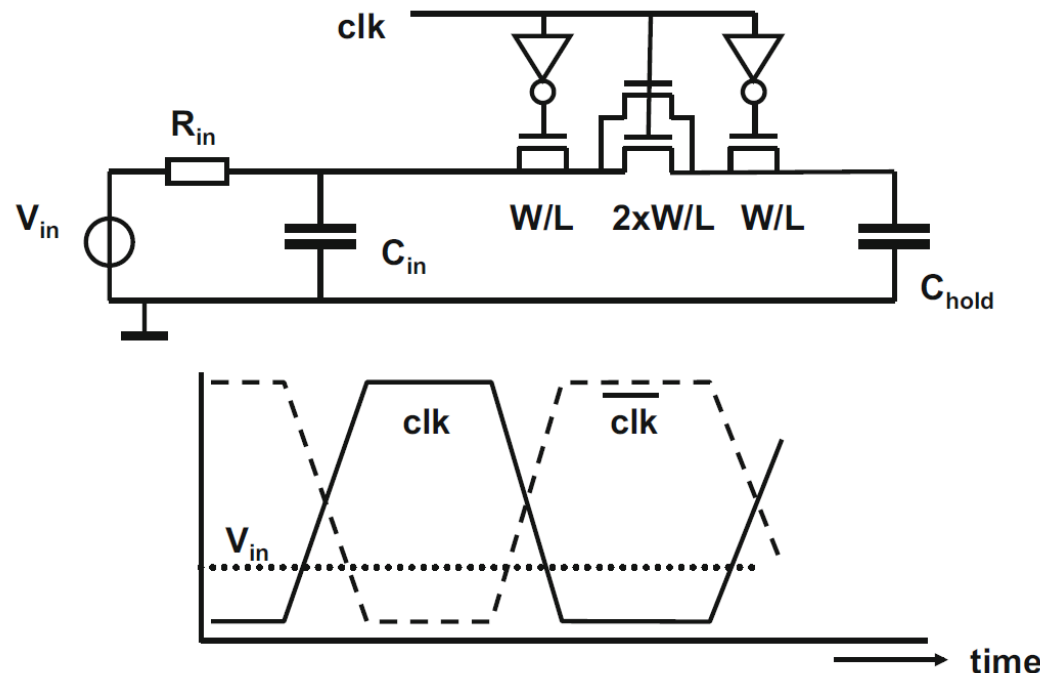- ❑ Switch charge injection (CI) error can be mitigated by using dummy switches
- ❑ The nonlinear dependence of CI on R_{in} , C_{hold} , and clock rise/fall time makes it difficult to achieve a precise cancellation
- ❑ clk rising edge must trail \overline{clk} falling edge




Bottom-Plate Sampling Principle

  - Add another switch at the bottom plate
 - The new switch charge injection is independent of V_{in}
 - No non-linear error \rightarrow No distortion
 - Necessary for more than 8-bit resolution




T/H Errors (2)

 - ❑ Aperture delay – the delay Δt between hold command and hold action
- ❑ Aperture jitter – the random variation in Δt (i.e., sampling clock jitter)



Signal-Dependent Aperture Delay

 - ❑ Non-uniform sampling due to signal-dependent aperture delay causes distortion in top-plate S/H
- ❑ Sharp clock edge and small V_{in} mitigate the delay variation





$$V_i(t) = A \sin(\omega t)$$

$$V_o(t) = A \sin \left[\omega \left(t - \frac{V_i(t)}{SR} \right) \right]$$


Transmission Gate (TG)

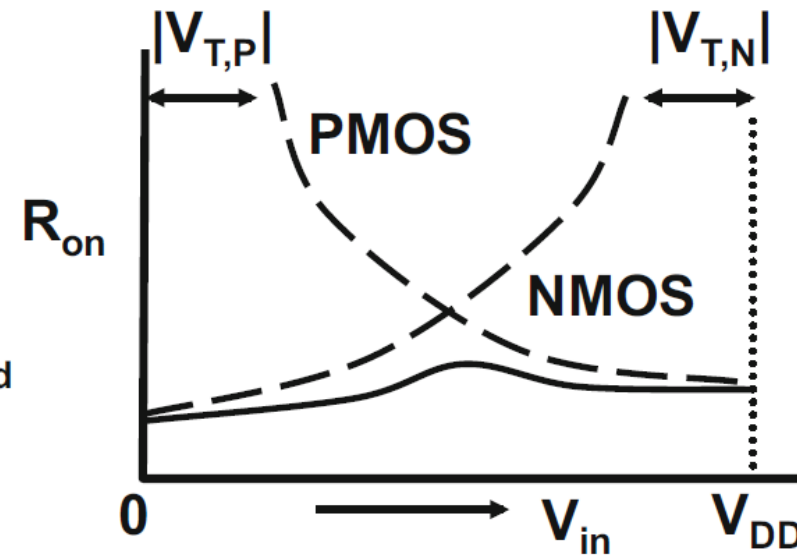 - ❑ R_{on} (and TBW) depends on V_{in}
 - Can be reduced by using CMOS switch (TG)
 - May be indispensable for low voltage operation
- ❑ Delay mismatch between clk and \overline{clk} will cause distortion error




Bootstrapping Principle

 - ❑ Pros: $V_{GS} = \text{constant} = V_{DD}$
 - Less R_{on} variation with $V_{in} \rightarrow$ Better linearity and TBW
 - No need for TG (avoids PMOS large cap and parasitics)
 - Use smaller NMOS switch (less clock loading)
- ❑ Cons
 - Complexity, area, and power (see next slides)
 - Device reliability (voltages above V_{DD} and/or below GND)
 - Residual error due to body effect




Bootstrapping Example (1)

 - Hold Mode: $\Phi = 0$
 - C is precharged




Bootstrapping Example (2)

 - Track mode: $\Phi = 1$
 - $V_{GS} = \text{constant} = V_{DD}$



Bootstrapping Example (3)

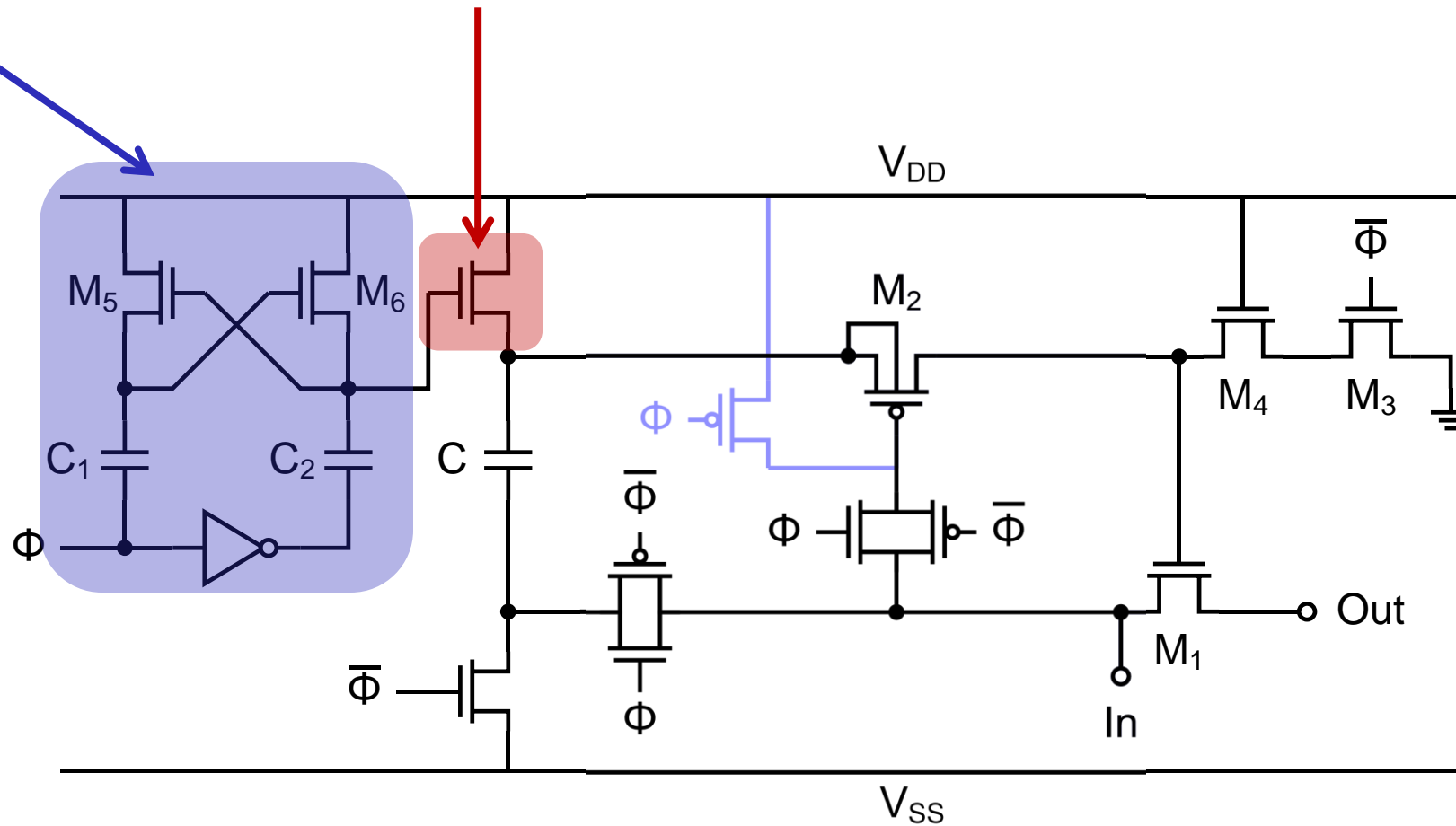
- ❑ Charge pump to drive the NMOS switch with $V_G > V_{DD}$



Sampling Jitter

- ❑ Jitter causes sample moments to shift from their position.
 - Can be viewed as noise in the time domain.

Part	Description	Jitter
“2011”	Quartz 50–170 MHz	3 ps _{rms}
“8002”	Programmable oscillator	25 ps _{rms}
“1028”	MEMS+PLL combi 100 MHz	95 ps _{rms}
“6909”	RC oscillator 20 MHz	0.2 %
“555”	RC oscillator/timer	> 50 ns _{rms}

 

Jitter vs Phase Noise (1)

- Variations in time (jitter) is equivalent to variations in phase (phase noise)

$$V_s = V_o \sin(\omega_s t) = V_o \sin(\theta)$$

$$\theta = \omega_s t = 2\pi f_s t$$



$$\frac{\theta}{2\pi} = \frac{t}{T_s}$$

$$\frac{\Delta\theta}{2\pi} = \frac{\Delta t}{T_s}$$

$$\frac{\sigma_{\theta,rms}}{2\pi} = \frac{\sigma_{t,rms}}{T_s}$$

Jitter vs Phase Noise (2)

  - ❑ Jitter in time domain is equivalent to Phase Noise in frequency domain.
- ❑ Jitter terminology usually used in sampled systems.
- ❑ Phase noise terminology usually used in RF systems.
 - Noise density is measured at an offset (f_m) w.r.t. the carrier frequency.
- ❑ BPF can reduce jitter levels to around 0.1 psrms.



Jitter Limited SNR (1)

- ❑ Timing variations means amplitude variations
- ❑ Jitter limits the max attainable SNR


$$A(nT_s + \Delta t(t)) = \hat{A} \sin(\omega \times (nT_s + \Delta t(t)))$$

$$\Delta A(nT_s) = \frac{d\hat{A} \sin(\omega t)}{dt} \times \Delta t(nT_s) = \omega \hat{A} \cos(\omega nT_s) \Delta t(nT_s)$$

$$\sigma_A^2(nT_s) = \left(\frac{dA(nT_s)}{dt} \right)^2 \sigma_t^2 = \omega^2 \hat{A}^2 \cos^2(\omega nT_s) \sigma_t^2$$

$$\sigma_A^2 = \frac{\omega^2 \hat{A}^2 \sigma_t^2}{2}$$

 
$$\text{SNR} = \frac{P_{\text{signal}}}{P_{\text{jitter}}} = \frac{\hat{A}^2/2}{\sigma_A^2} = \left(\frac{1}{\omega \sigma_t} \right)^2 = \left(\frac{1}{2\pi f \sigma_t} \right)^2$$



Jitter Limited SNR (2)

$$\text{SNR} = 20^{10} \log \left(\frac{1}{\omega \sigma_t} \right) = 20^{10} \log \left(\frac{1}{2\pi f \sigma_t} \right)$$

 - ❑ Jitter can be a limiting factor for high-speed ADCs.



T/H Performance Summary

$$\text{SNDR} = \frac{\overline{V_i^2}}{\overline{V_N^2} + \frac{A^2 \omega^2}{2} \overline{\delta t^2} + \overline{V_\epsilon^2}}$$

Noise Jitter Distortion

References

- ❑ M. Pelgrom, Analog-to-Digital Conversion, Springer, 3rd ed., 2017.
- ❑ W. Kester, The Data Conversion Handbook, ADI, Newnes, 2005.
- ❑ B. Boser and H. Khorramabadi, EECS 247 (previously EECS 240), Berkeley.
- ❑ B. Murmann, EE 315, Stanford.
- ❑ Y. Chiu, EECT 7327, UTD.

Course Resources

Lectures



Labs



YouTube Channel



Thank you!