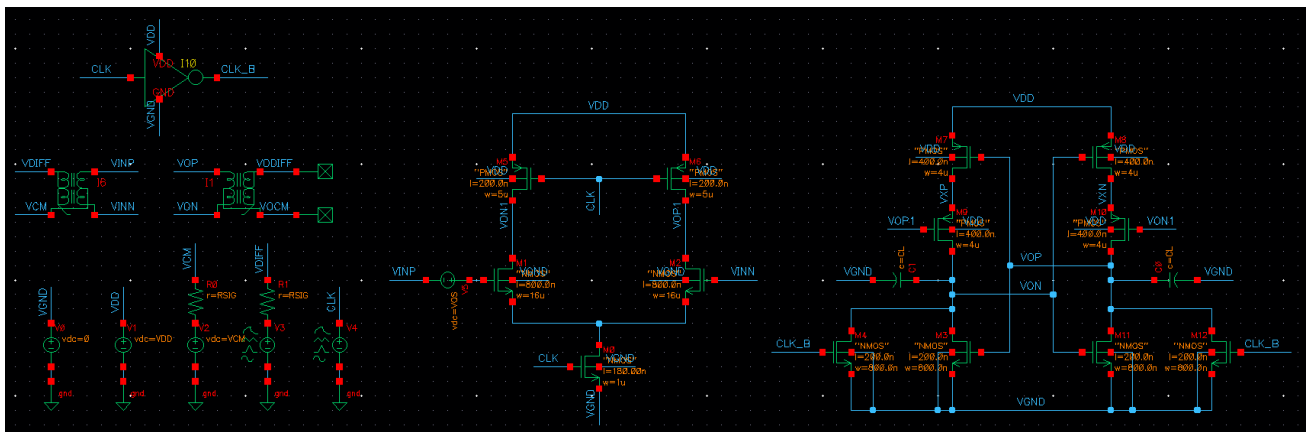


**Analog Integrated System Design – Cadence Tools****Lab 07****Dynamic Comparator****Intended Learning Objectives**

- 1) To be familiar with the operation of dynamic comparator.
- 2) To be familiar with the simulation and characterization of dynamic comparator.

**PART 1: Basic Dynamic Comparator Simulation**


- 1) Carefully read the description of the dynamic comparator reported in the following paper:  
P. Harpe *et. al.*, A 26 uW 8 bit 10 MS/s asynchronous SAR ADC for low energy radios, Solid-State Circuits, IEEE Journal of, 2011, 46, 1585-1595
- 2) Create a testbench for the above-mentioned dynamic comparator. Scale the sizing of the transistors to meet your technology minimum channel length.




- 3) Set the clock as follows: one value (initial) = 0, zero value (pulse) = VDD, period = TCLK, rise/fall time = TRF, delay = TCLK/2, pulse width = TCLK/2. The remaining sources are simple DC sources.
- 4) The differential input signal is set as DC source (we will apply different stimuli in the next parts).
- 5) Set the global variables as below.

CL	50f
TCLK	20n
TRF	100p
RSIG	100
VOS	0
VDD	2
VCM	VDD/2
VDIFF	10m

 - 6) Run transient simulation for  $2 \times \text{VAR}(\text{"TCLK"})$  conservative. Examine the transient waveforms at different points of the design.
- 7) Calculate the delay using the calculator.  
`delay(?wf1 VT("/CLK") ?value1 1.0 ?edge1 "rising" ?nth1 1 ?td1 0.0 ?wf2 abs(VT("/VODIFF")) ?value2 1.0 ?edge2 "either" ?nth2 1 ?td2 nil ?stop nil ?multiple nil)`
- 8) Plot the power consumption vs time. Calculate the average power consumption using the calculator.  
`VAR("VDD")*average(IT("/V1/MINUS"))`
- 9) Set a logarithmic parametric sweep for the differential input voltage. Set VDIFF = 100uV to 100mV, 10 steps, logarithmic.
- 10) Run transient analysis and plot the delay vs VDIFF. Use log axis for VDIFF. Comment on the results.



 - 11) Set VDIFF to its original value. Set TCLK = 1/FCLK and set a linear sweep for FCLK 10M:10M:50M. Plot the average power consumption vs FCLK. Comment on the results.




## PART 2: Overdrive (Overload) Recovery Test

- 1) We will apply small input ( $\pm 0.5$  LSB) is applied to the comparator input in a cycle right after a full-scale input is applied; the comparator should be able to resolve to the right output in either case → memoryless.
- 1) Change the differential input to be a pulse source with the following parameters: one value (initial) = VREFP, zero value (pulse) = VTEST, period =  $2 \cdot \text{TCLK}$ , rise/fall time = TRF, delay = 0, pulse width = TCLK.
- 2) Assume the comparator will be used in an 8-bit ADC. Set global parameters as shown below.

CL	50f
TCLK	20n
TRF	100p
RSIG	100
VOS	0
VDD	2
VCM	$0.5 \cdot (\text{VREFP} + \text{VREFN})$
VDIFF	10m
VREFP	$0.75 \cdot \text{VDD}$
VREFN	$0.25 \cdot \text{VDD}$
NBIT	8
VLSB	$(\text{VREFP} - \text{VREFN}) / 2^{**} \text{NBIT}$
VTEST	$\text{VLSB}/2, -\text{VLSB}/2$

 - 3) Run transient analysis and plot the output for the two extreme cases.



## PART 3: Offset Voltage Simulation

- 1) We will create two Verilog-A models to help in offset voltage simulation<sup>1</sup>. Read and analyze the code below. The first model is an ideal sample and hold. The second model samples the offset voltage and stops the simulation afterwards.

```
`include "constants.vams"
`include "disciplines.vams"
// sah_ideal
// ideal sample and hold amplifier
//
module sah_ideal(vin, vout, vclk);
input vin, vclk;
output vout;
electrical vin, vout, vclk;
parameter real vth = 1;      // set it to VDD/2
real vout_val;

    analog begin
        @ (cross(V(vclk) - vth, 1.0) or initial_step)
            vout_val = V(vin);
            V(vout) <+ vout_val ;
    end
endmodule
```

```
`include "constants.vams"
`include "disciplines.vams"

module vos_sampling(vin_diff, vout_diff, vos);
input vin_diff, vout_diff;
output vos;
electrical vin_diff, vout_diff, vos;

parameter real TCLK = 20n;
parameter real VDD = 2.0;

// real variables are automatically initialized to zero
real vin_diff_delayed;
real vos_val;
integer done;

    analog begin


        @(initial_step) done = 0;

        vin_diff_delayed = absdelay(V(vin_diff), TCLK/4);

        // Do not use the `cross' analog operator in a conditionally-executed statement or
in an expression
        @ (cross(V(vout_diff) - VDD/2, +1)) begin
            if (done == 0) begin
                vos_val = -vin_diff_delayed;
                done = 1;
            end
            else begin
                done = 2;
            end
        end
        V(vos) <+ vos_val ;
        if (done == 2) $finish_current_analysis;
    end
endmodule
```

<sup>1</sup> A fast and accurate technique for comparator offset voltage simulation is reported here: Hesham Omran, Fast and accurate technique for comparator offset voltage simulation, Microelectronics Journal, Volume 89, 2019, Pages 91-97.

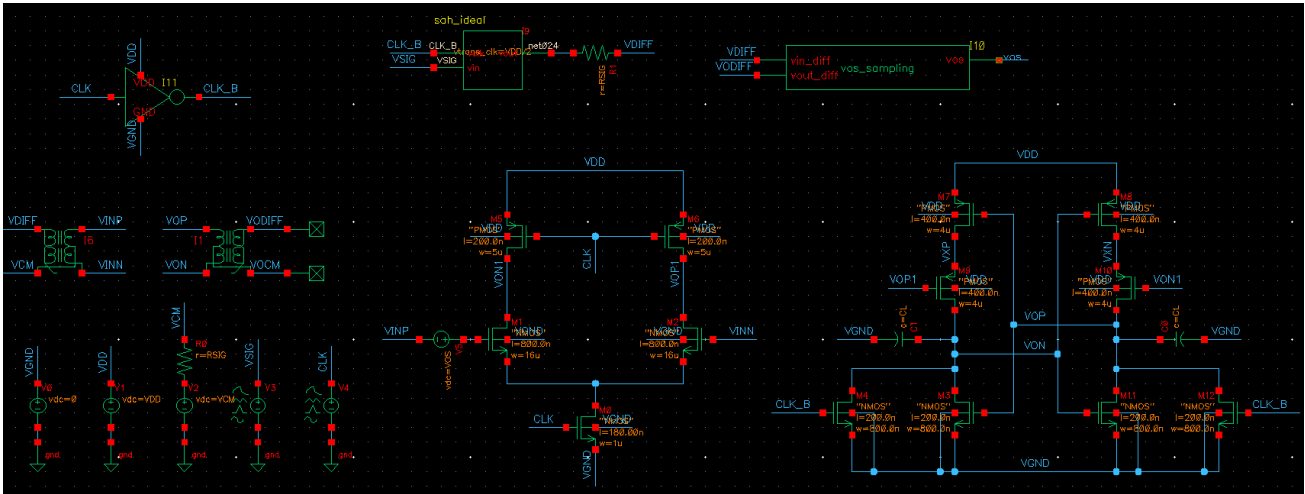- 2) Copy the testbench to a new one and modify it as below. Practically Monte Carlo simulation should be used to simulate the offset voltage. But we artificially add an offset voltage using vdc source as a simple test case.



- 3) Set the input signal to be a PWL source: (0, -VDIFF) (NPTS\*TCLK, VDIFF)
- 4) Set global variables as shown below. Set the properties of the Verilog-A blocks as a function of the global variables.

CL	50f
TCLK	20n
TRF	100p
RSIG	100
VOS	5.4m
VDD	2
VCM	VDD/2
VDIFF	10m
NPTS	100

- 5) Run conservative transient analysis with  $tstop = \text{VAR}("NPTS") * \text{VAR}("TCLK")$ .
- 6) Use the following expression in the calculator to evaluate the offset voltage.  
 $\text{value}(\text{VT}("/\text{vos}") \text{ ymax}(\text{xval}(\text{VT}("/\text{vos}"))))$
- 7) Compare the evaluated offset with the value added in the global variables.