

Analog Integrated Systems Design


Lecture 11 Comparators

Dr. Hesham A. Omran


Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Comparator

 - ❑ The comparator circuit is the location where the digital decision is made
 - “Where nature turns into bits”
- ❑ Detects the polarity of a differential analog input signal
 - Generates a digital output (1 or 0) accordingly
- ❑ Or compares a SE input to a threshold (reference) voltage
 - Threshold-crossing detector




Circuit symbol

 

Transfer characteristic
(ideal)

Comparators in ADCs

 - ❑ Every analog-to-digital converter contains at least one comparator
- ❑ There are many different comparator implementations
 - There is NO universal “one design fits all” comparator
- ❑ Main design trade-off: accuracy and speed vs power consumption




Comparator Requirements

- ☐ Large amplification (fine resolution / high sensitivity)
 - Needs to translate mV or uV differential input to '0' and '1'
- ☐ Wide bandwidth (high speed)
- ☐ Accuracy
 - Low input offset and low noise
- ☐ Low power consumption
- ☐ No memory (hysteresis)
 - Previous comparator decision should not affect the following
- ☐ No metastability
 - Any decision is better than no decision!
- ☐ Wide common mode input range
- ☐ High CMRR

Comparator Topologies


- Straight-forward amplification

- Simple
- Relatively slow

 

❑ Latch comparator

 
- **A.k.a. clocked / dynamic / regenerative comparator**
- **Clock is required**
- **Built-in S/H**



Regeneration Example



Pre-amplification

- ❑ A pre-amplifier is used before the regenerative section of the comparator is activated
 - Reduces the influence of mismatch in the regenerative section
 - Creates a form of isolation between the regeneration process and the input sources
 - No reason to boost the DC-gain to very high values (usually ≤ 10)
 - Low gain allows operations at high speed (large bandwidth)
 - Just sufficient to suppress latch mismatch and noise
- ❑ Most comparators use an input differential pair as a pre-amplifier

 


Regenerative Comparator Example

  - ❑ After some amplification, a positive feedback latch activated by a clock pulse will turn the latch on
 - The latch will amplify the small input voltage difference to a large signal



Regenerative Latch Delay

 



Regenerative Latch Delay

- Assume the pre-amplified latch input voltage = $\Delta V_{in} = \alpha V_{LSB}$ ($0 < \alpha < 1$)

$$\tau \approx \frac{C}{g_{m,l}}$$

$$V(t) = \Delta V_{in} e^{+t/\tau}$$

  
- The exponential signal growth makes a latch a fast decision element in a regenerative comparator
- The exponential growth will continue until some non-linear limiting mechanism takes action (e.g., approaching power rails)



Comparator Delay Example


- ❑ The time a comparator or latch needs to form a digital signal depends on the initial over-drive voltage
 - The input differential voltage determines the delay of the comparator
 
$$V(t) = \Delta V_{in} e^{+t/\tau} \rightarrow t_d = \tau \ln \frac{V_{FS}}{\Delta V_{in}} = \tau (\ln V_{FS} - \ln \Delta V_{in})$$



Metastability

 - ❑ For very small overdrive voltages, the comparator cannot reach a decision in the limited time of a half clock period (T_S)
- ❑ The comparator will not generate a clear “zero” or “one” output level after time T_S
- ❑ The succeeding logical circuitry will behave ambiguously



Bit-Error Rate (BER)

- ❑ Assume the pre-amplified latch input voltage = αV_{LSB} ($0 < \alpha < 1$)
- ❑ Assume ambiguity happens when $V(T_S) < V_{FS}$

$$V(T_S) = \alpha V_{LSB} e^{+T_S/\tau} < V_{FS}$$

$$\alpha_{min} = \frac{V_{FS}}{V_{LSB}} e^{-T_S/\tau} = 2^N e^{-T_S/\tau}$$

- ❑ Assume V_{in} is uniformly distributed: $0 < \alpha < 1$

$$BER = \alpha_{min} = 2^N e^{-T_S/\tau}$$

Bit-Error Rate (BER)

- Assume V_{in} is uniformly distributed: $0 < \alpha < 1$

$$BER = \alpha_{min} = 2^N e^{-T_s/\tau}$$

- From a fundamental point of view the BER cannot be avoided completely
 - But can be made very small (10^{-13} is possible)
- Measures to improve the BER include:
 - Improving the latch speed with more current and smaller capacitances
 - Additional gain stages or a second latch
 - $\Delta V_{in} = \alpha V_{LSB}$ larger than V_{LSB} ($0 < \alpha < A$, where $A > 1$)
 - Using special decoding scheme to avoid large code errors in case of a metastable state


Comparator Offset Voltage

- ❑ In some types of ADCs the static random offset just generates a (random) DC-shift of the entire signal → offset error
- ❑ In other types of ADCs the input referred random offset is crucial because it impacts both INL and DNL
 - $0.5\text{LSB} > 3\sigma_{in,os}$


Static vs Dynamic Offset

- ❑ Offset voltage has static and dynamic components
 - Static offset:
 1. Systematic offset (due to systematic mismatch): can be minimized by good design and matched layout
 2. Random offset (due to random mismatch): reduced by using large devices but cannot be eliminated (Pelgrom's model)
 - Static offset is dominant in preamplifiers
 - Dynamic offset:
 - Due to imbalanced switching effects and capacitive load mismatch
 - Dynamic offset is dominant in latches

Multistage Preamplifier Offset

 

Individual stage

 


Total input-referred

$$A_T = A_1 \cdot A_2 \cdot A_3$$
$$V_{os} = V_{os1} + \frac{V_{os2}}{A_1} + \frac{V_{os3}}{A_1 \cdot A_2}$$

Comparator Static Offset

 
$$\sigma_{V_{in}}^2 = \sigma_{V_{T,12}}^2 + \frac{g_{m,34}^2}{g_{m,12}^2} \sigma_{V_{T,34}}^2 + \frac{I_{load}^2}{g_{m,12}^2} \frac{\sigma_R^2}{R_{1,2}^2}$$



Latch Dynamic Offset


- ❑ M5-6: input pair
- ❑ M7-8: cross-coupled load (regenerative)
- ❑ M9: reset switch

 - ❑ Dynamic offset due to:
 - Imbalanced CI and CF
 - Imbalanced load capacitance
 - Mismatch between M_5 and M_6
 - Mismatch between M_7 and M_8
 - Clock routing




Input Offset Cancellation

 - ❑ AC coupling at input with input-referred offset stored in C
- ❑ Two-phase operation
 - Phase (Φ_2) is used to store offset



Input Offset Cancellation

 
- ❑ Offset Storage Phase – Φ_2
 - Closed-loop stability required (amplifier in unity-gain feedback)



Ref: J. L. McCreary and P. R. Gray, "All-MOS charge redistribution analog-to-digital conversion techniques. I," *JSSC*, vol. 10, pp. 371-379, issue 6, 1975.

Input Offset Cancellation

 - Amplifying Phase – Φ_1
 - Offset cancellation is incomplete if A is finite
 - Input AC coupling attenuates signal gain





$$\begin{aligned} V_o &= -A(V_{in} + V_c - V_{os}) \\ &= -A\left(V_{in} - \frac{V_{os}}{1+A}\right) \end{aligned}$$

Input - referred offset :

$$V_{os,in} = \frac{V_{os}}{1+A}$$


Input Offset Cancellation

  - Fully differential operation to mitigate charge injection and clock feedthrough errors.
 - Necessary for any high precision switched-capacitor integrated circuits




Output Offset Cancellation

 - ❑ AC coupling at output with offset stored in C
- ❑ The gain (A) must be small and stable (independent of V_o)
- ❑ Does not work for high-gain amplifier



Output Offset Cancellation

 - ❑ Offset Storage – Φ_2
 - Closed-loop stability is not required
 - CF (clock feedthrough) and CI (charge injection) of Φ_2' gets divided by A when referred to input




Ref: R. Poujois and J. Borel, "A low drift fully integrated MOSFET operational amplifier," JSSC, vol. 13, pp. 499-503, issue 4, 1978.

Output Offset Cancellation

□ Amplifying Phase – Φ_1

 - Cancellation is complete if A is constant (independent of V_o)
- AC coupling at output attenuates signal gain



$$\begin{aligned} V_o &= A(V_i - V_{os}) + AV_{os} \\ &= AV_{in} \end{aligned}$$



Input-referred offset:


$$V_{os,in} = 0$$

Comparator Noise

- ❑ The input referred noise voltage acts as time varying input offset
- ❑ If the thermal noise dominates:


$$v_{nout,rms}^2 = v_{nin}^2(f) \times A_v^2 \times B_N = \frac{4kT\gamma_{eff}}{g_m} \times A_v^2 \times B_N$$
$$v_{nin,rms} = \sqrt{\frac{4kT\gamma_{eff}}{g_m} \times B_N}$$

 - ❑ Trade-off between noise, speed, and power consumption




Quiz: Offset and Noise

 - Calculate the offset and noise from the shown measured comparator characteristics.




Kickback Noise

 - ❑ The output has sharp voltage transitions
- ❑ C_{gd} will pass these fast edges to V_{in} and V_{ref} causing “kickback”
 - Reference voltage disturbance must settle before next sample
- ❑ Reducing C_{gd} by reducing sizing will make mismatch worse
- ❑ The output swing can be reduced by using limiting circuits




Hysteresis

- ❑ Hysteresis: the comparator remembers its previous state.
- ❑ Either intentionally or as an unwanted consequence of the topology.
- ❑ Schmitt-trigger comparators use the hysteresis threshold to avoid unwanted transitions in case of noise signals
- ❑ The resolution of the comparator can be no less than the hysteresis
 - Large values of hysteresis are generally BAD for a high resolution comparator

 


Hysteresis Example

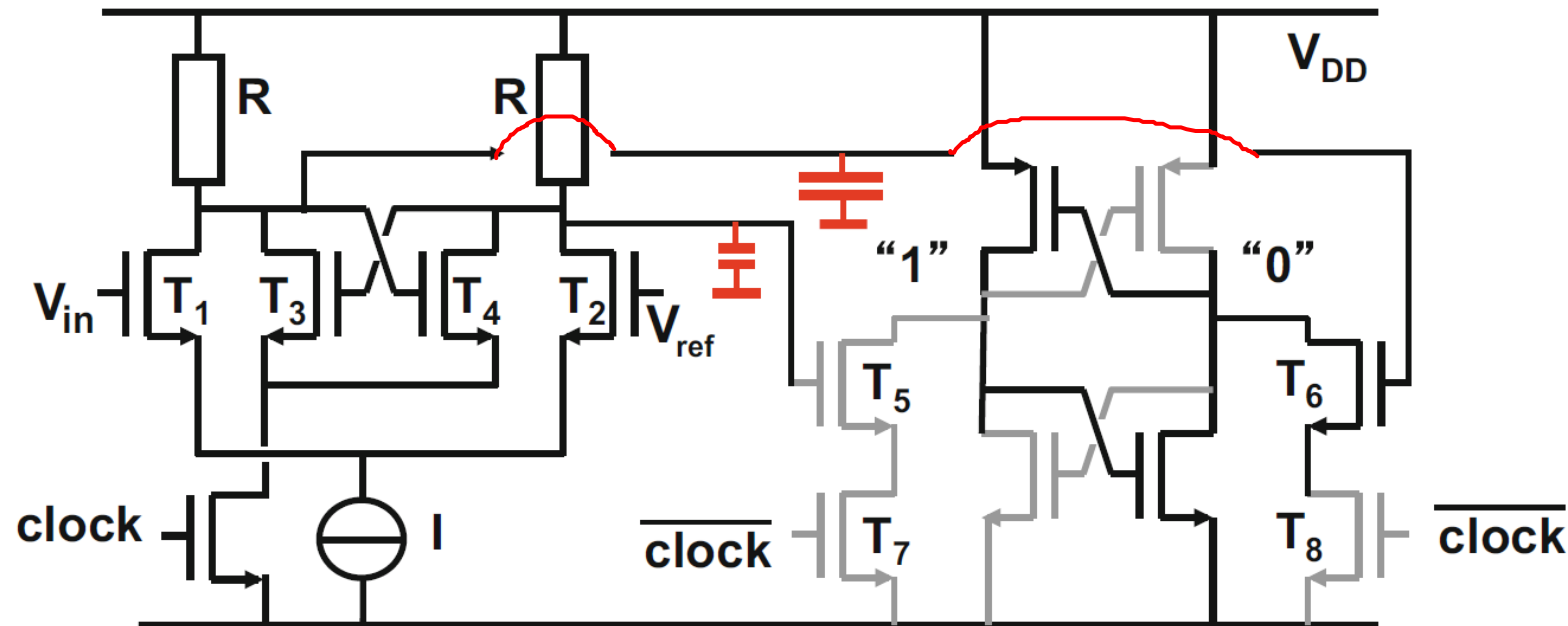- ❑ A pre-latch stage that is connected to a second stage consisting of a full digital latch activated by the inverse clock
- ❑ For the example below: ON transistor (T6) has much higher capacitance than T5
- ❑ The unequal capacitive loading favors a similar signal in the first latch → The consequence is a comparator with hysteresis.




Removing Hysteresis

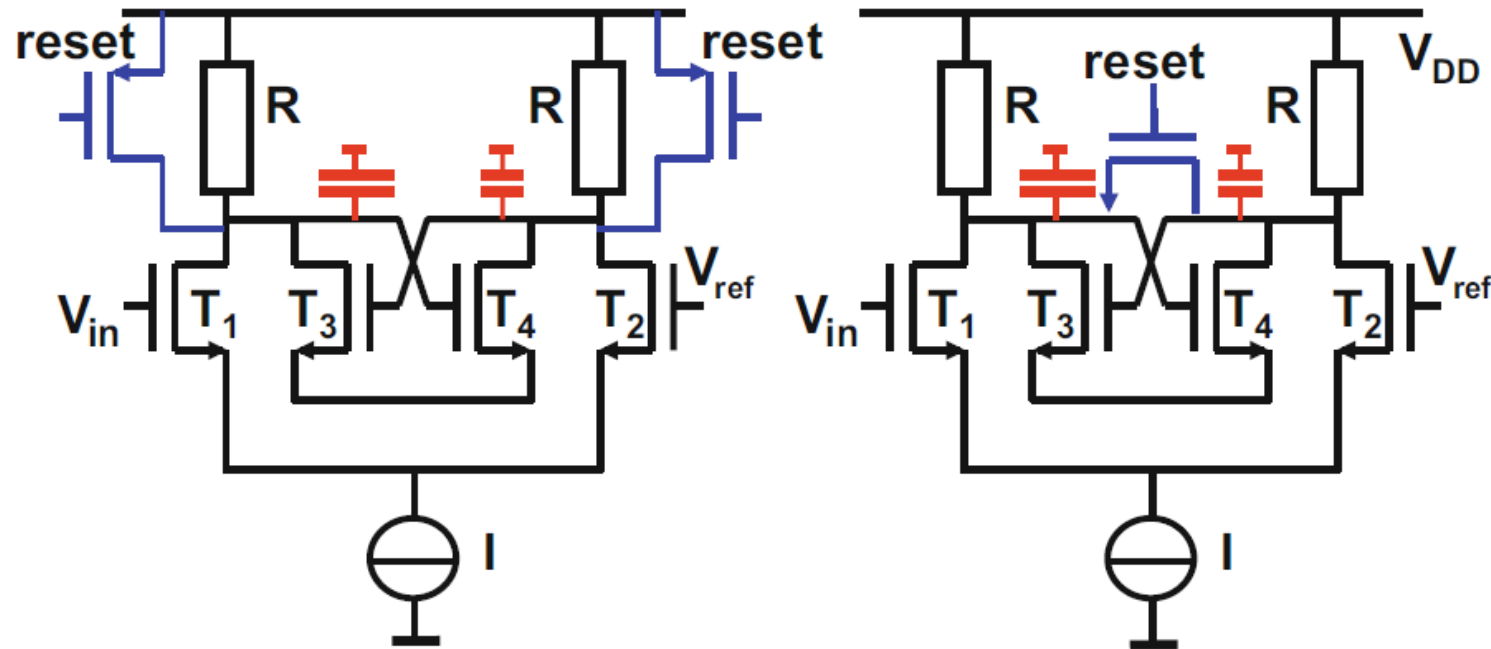- ❑ The previous state can be removed by resetting the latch in the comparator




Overdrive Recovery Test

- ❑ A small input (± 0.5 LSB) is applied to the comparator input in a cycle right after a full-scale input is applied
 - The comparator should be able to resolve to the right output in either case \rightarrow memoryless

 


Case I

 

Case II





The StrongArm Latch

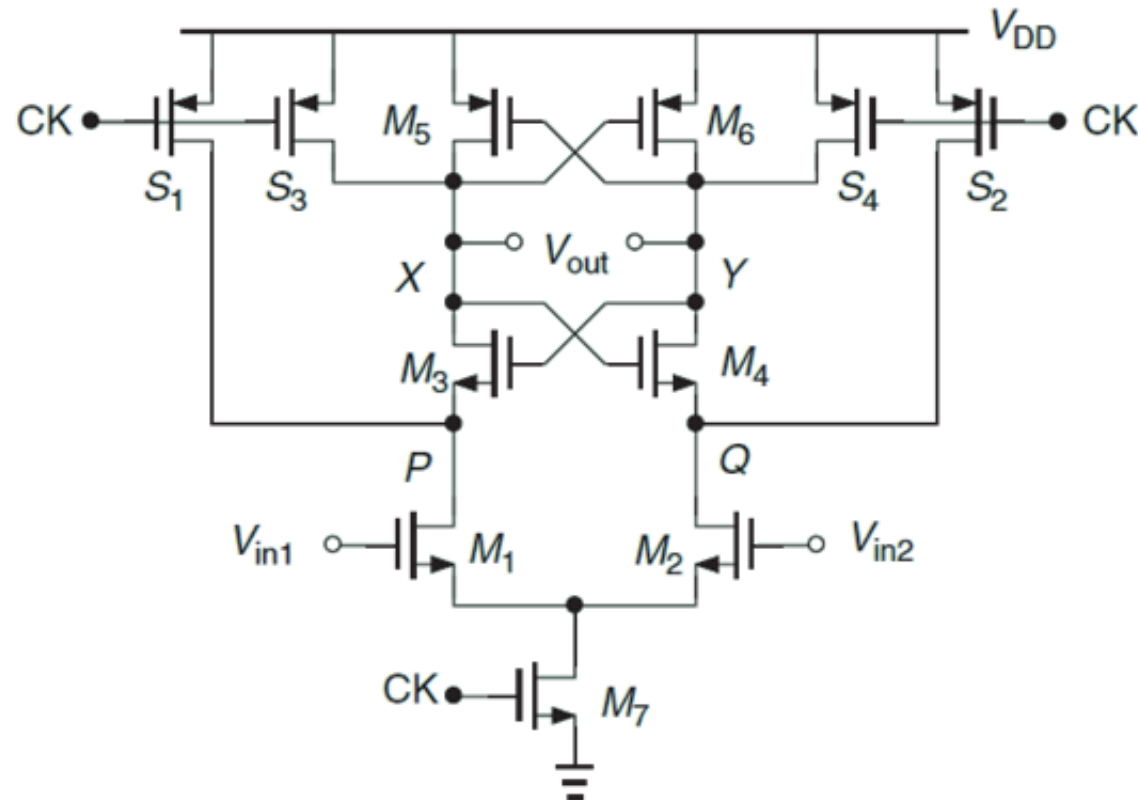- ❑ A popular latch design used in the StrongARM MPU in the 1990s
 - The input offset is relatively large (pre-amp or calib required)
 - Many modified versions exist






The StrongArm Latch

    - ❑ Precharge phase: $CK = 0$
- ❑ S1-4
 - Reset the latch and remove previous states (hysteresis)
 - Keep M3-6 initially off reducing their offset contribution
- ❑ Amplification phase: $CK = 1$






The StrongArm Latch

   - ❑ NMOS cross-coupled pair (M3,4) turns on
- ❑ M3,4 and M5,6 act as cross-coupled CMOS inverters
 - No static current flows




The StrongArm Latch

   - ❑ PMOS cross-coupled pair (M5,6) turns on
- ❑ Positive feedback brings one node to VDD and the other to GND






Fast Low-leakage Dynamic Comparator

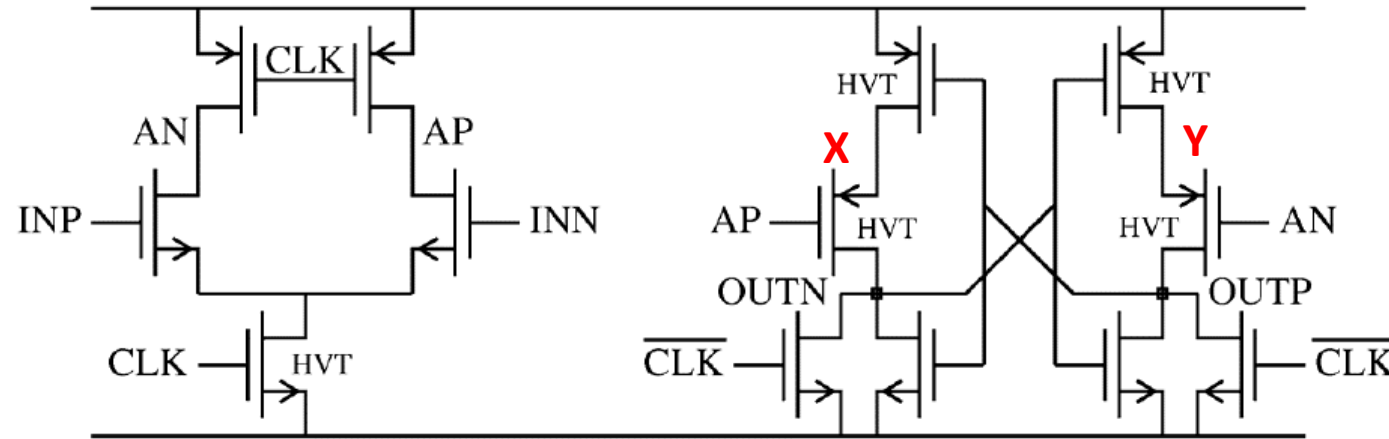- Comparator for low-power 8-bit SAR ADC (LSB = 3.2mV)



PMOS: 2.5u/0.1u
NMOS: 8u/0.4u (Diff. pair), 2.5u/0.2u (Tail switch)

PMOS: 2u/0.2u
NMOS: 0.4u/0.1u

   

References

- ❑ M. Pelgrom, Analog-to-Digital Conversion, Springer, 3rd ed., 2017.
- ❑ W. Kester, The Data Conversion Handbook, ADI, Newnes, 2005.
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” Wiley, 2nd ed., 2012.
- ❑ B. Boser and H. Khorramabadi, EECS 247 (previously EECS 240), Berkeley.
- ❑ B. Murmann, EE 315, Stanford.
- ❑ Y. Chiu, EECT 7327, UTD.

Thank you!